
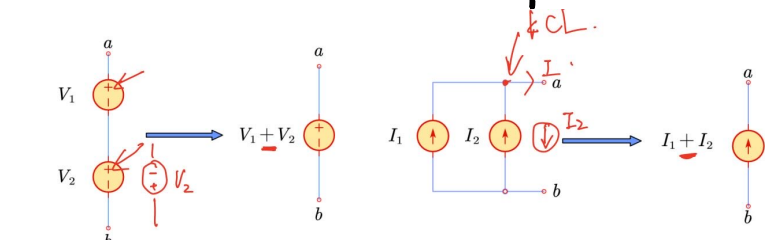


Source Combination (follows KCL & KVL)

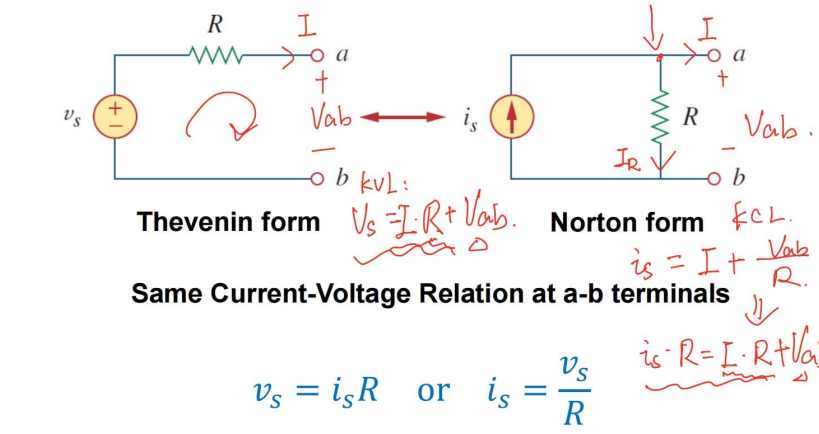


Source Transformation




Equivalent Circuit
a circuit having similar i-v characteristics

Node Method / loop Current Method

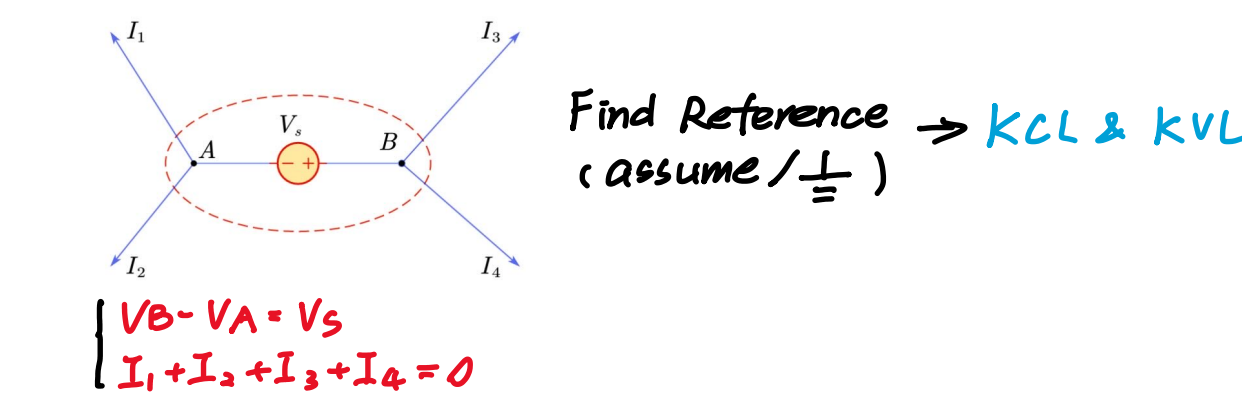

Superposition (Use Linearity)

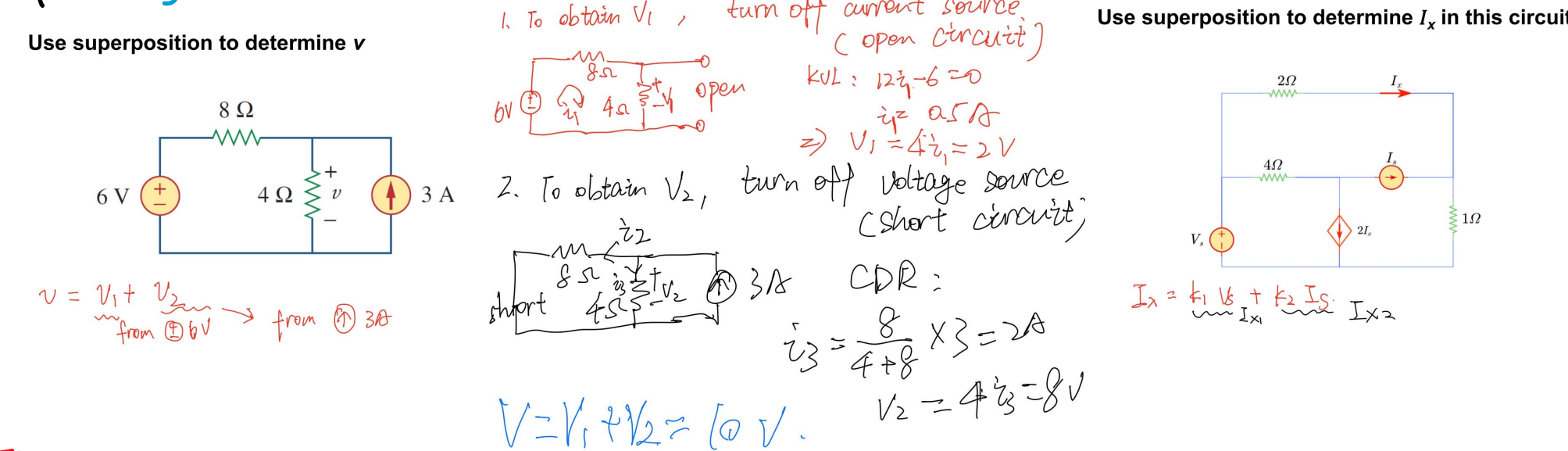
- Current Source → Open loop
- Voltage Source → Short Circuits



Thevenin & Norton Equivalent


Find $V_T \rightarrow$ Open circuit
 $I_N \rightarrow$ Short circuit
 $R_T = \frac{V_T}{I_N}$

Maximum Power Transfer

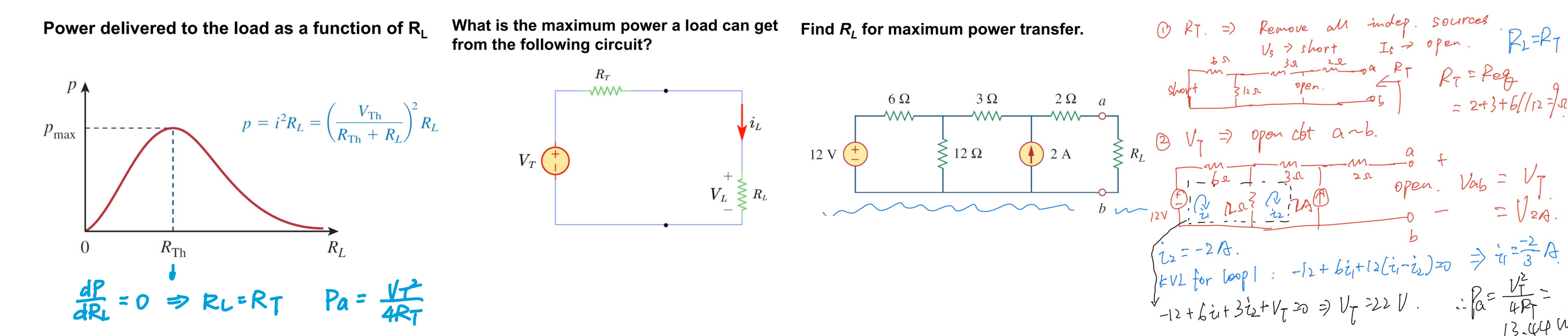


Signal Processing Circuit

Operational Amplifier (Op-Amp)

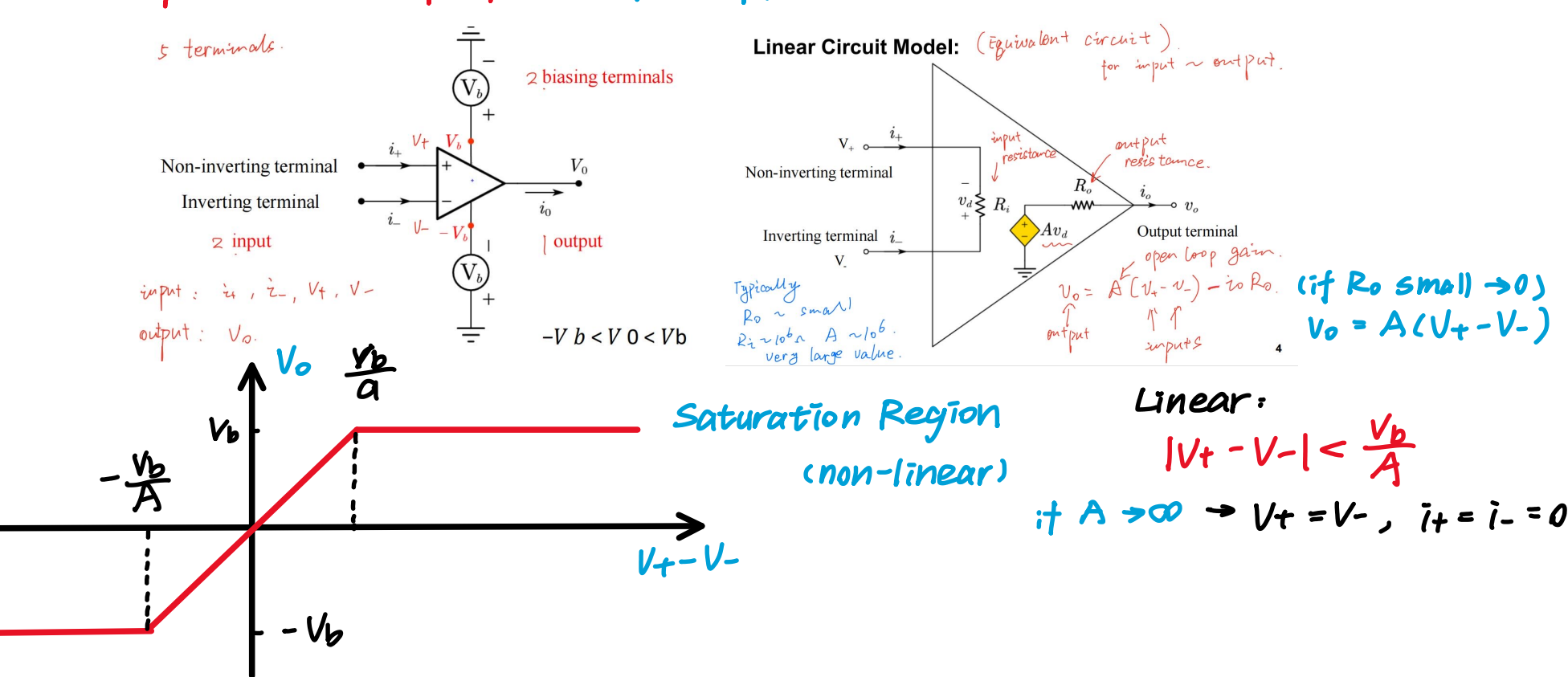

- Ideal Op-Amp: • Infinite open-loop gain ($A \rightarrow \infty$)
- Infinite input Resistance ($R_i \rightarrow \infty$)
- Zero Output Resistance ($R_o \rightarrow 0$)


Examples :

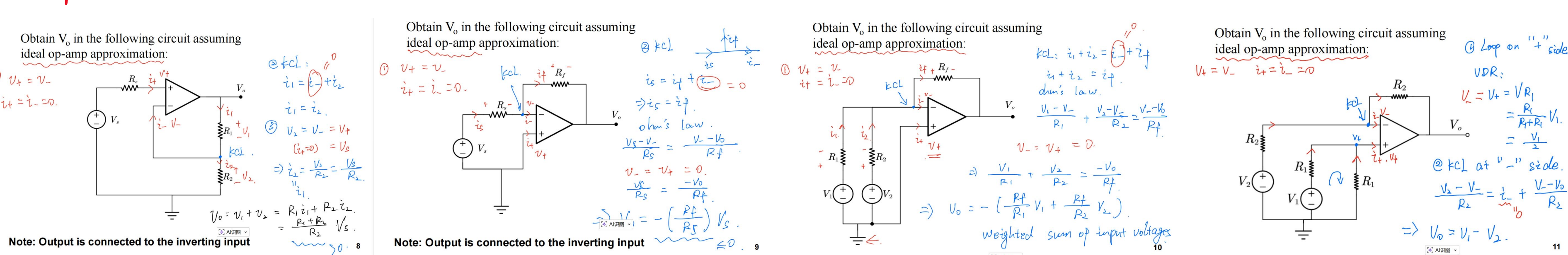


Ideal Circuit elements

$C: \frac{1}{C} \int i dt + \frac{1}{C} \int i dt = \frac{1}{C} \int i dt$
 $i = C \frac{dv}{dt}$
 $V(t) = \frac{1}{C} \int i dt$
 $L: \frac{1}{L} \int v dt + \frac{1}{L} \int v dt = \frac{1}{L} \int v dt$
 $v = L \frac{di}{dt}$
 $I(t) = \frac{1}{L} \int v dt$


Voltage Differentiator

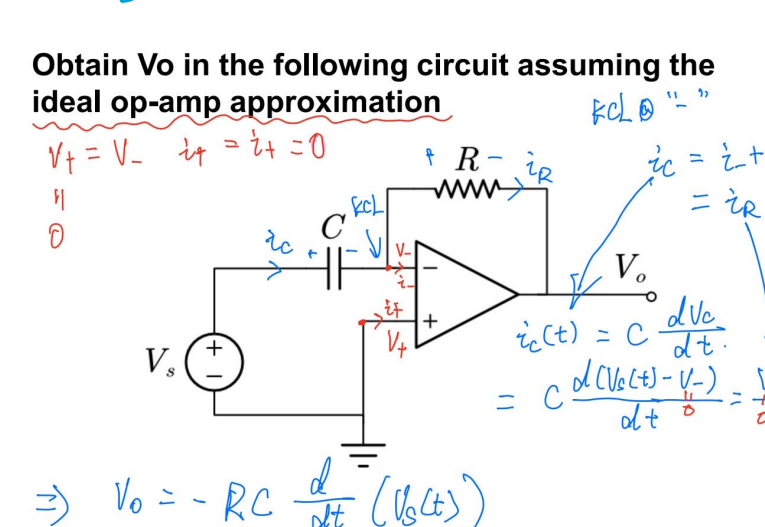


Adder Differentiator

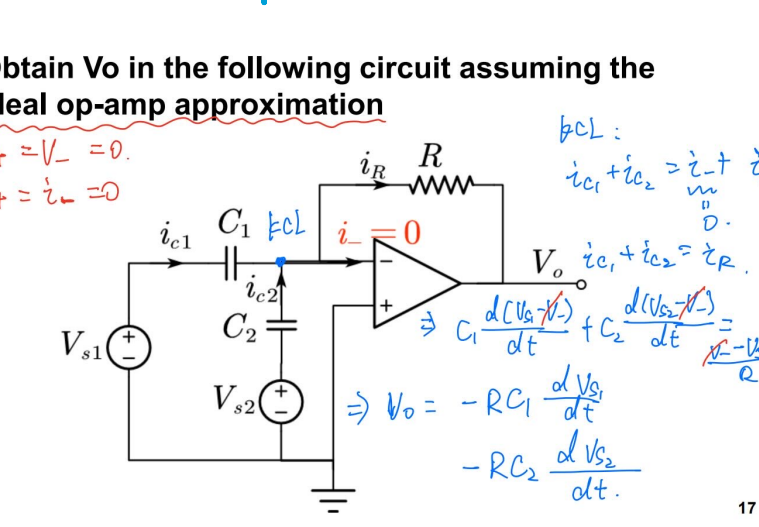


Voltage Integrator

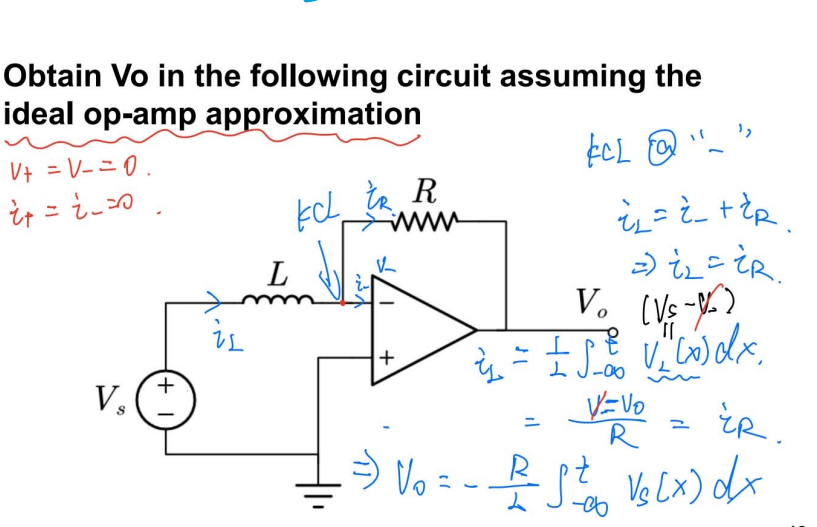


Integrator

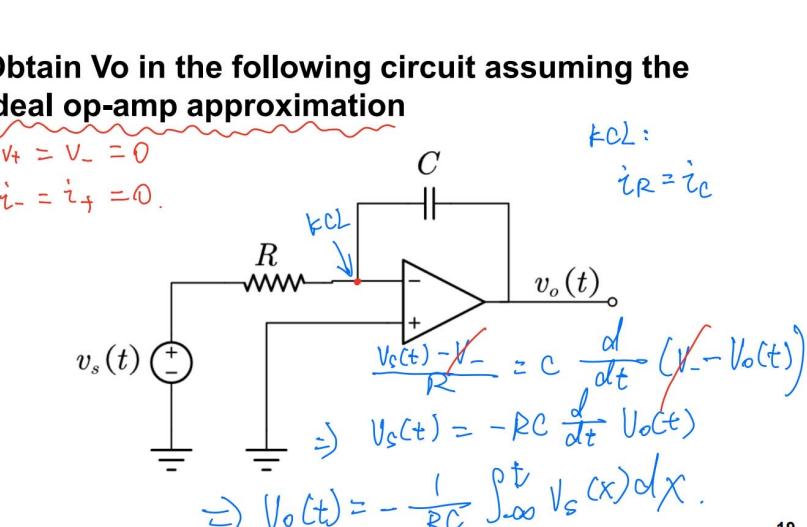


Linearity

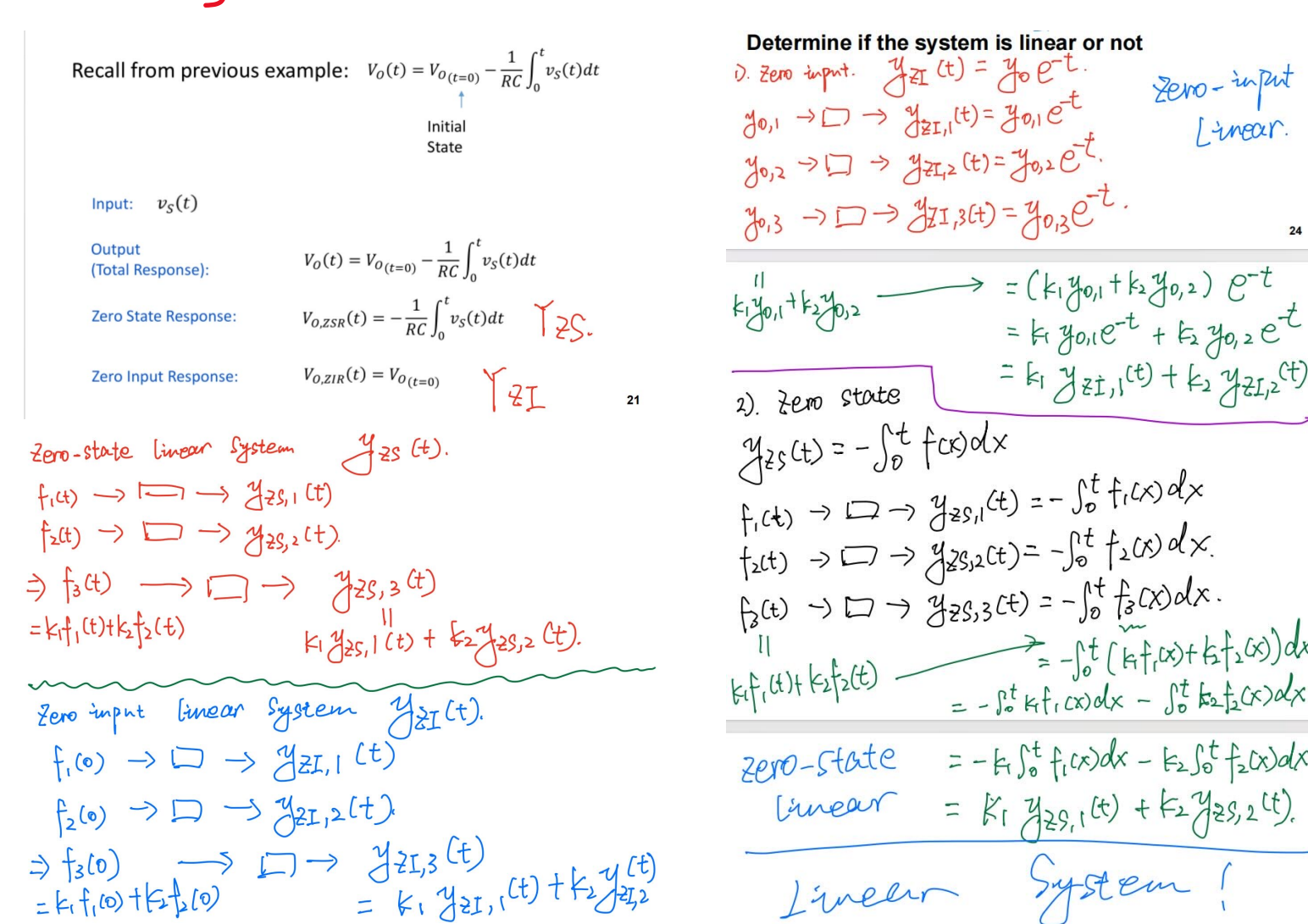


Time Invariance

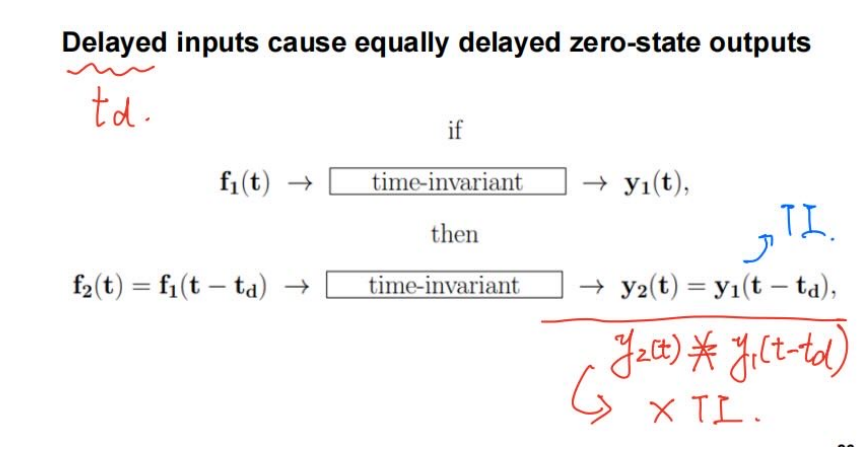


First-Order RC Circuit

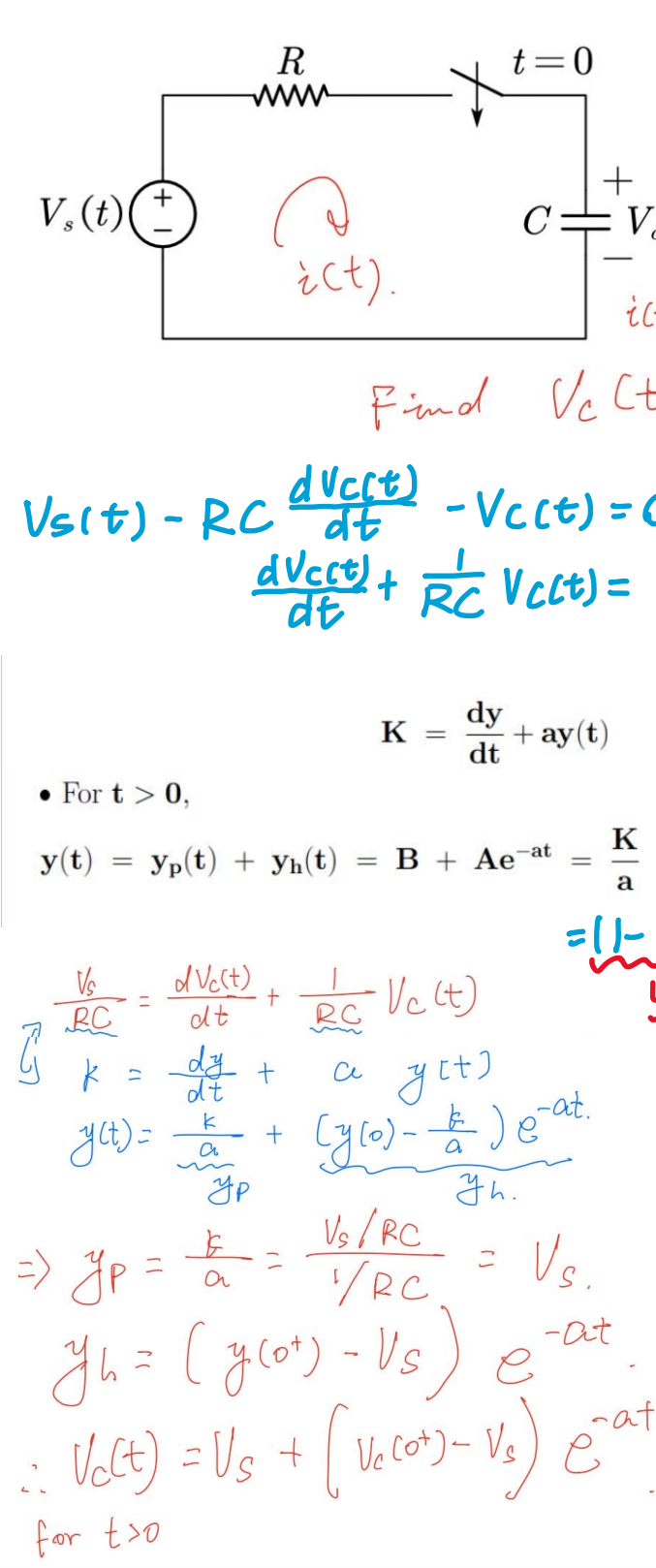

A Simple Solution Method

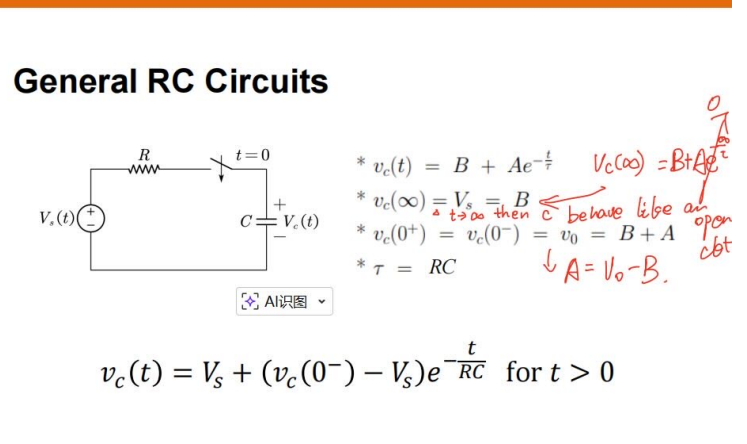

Example 1

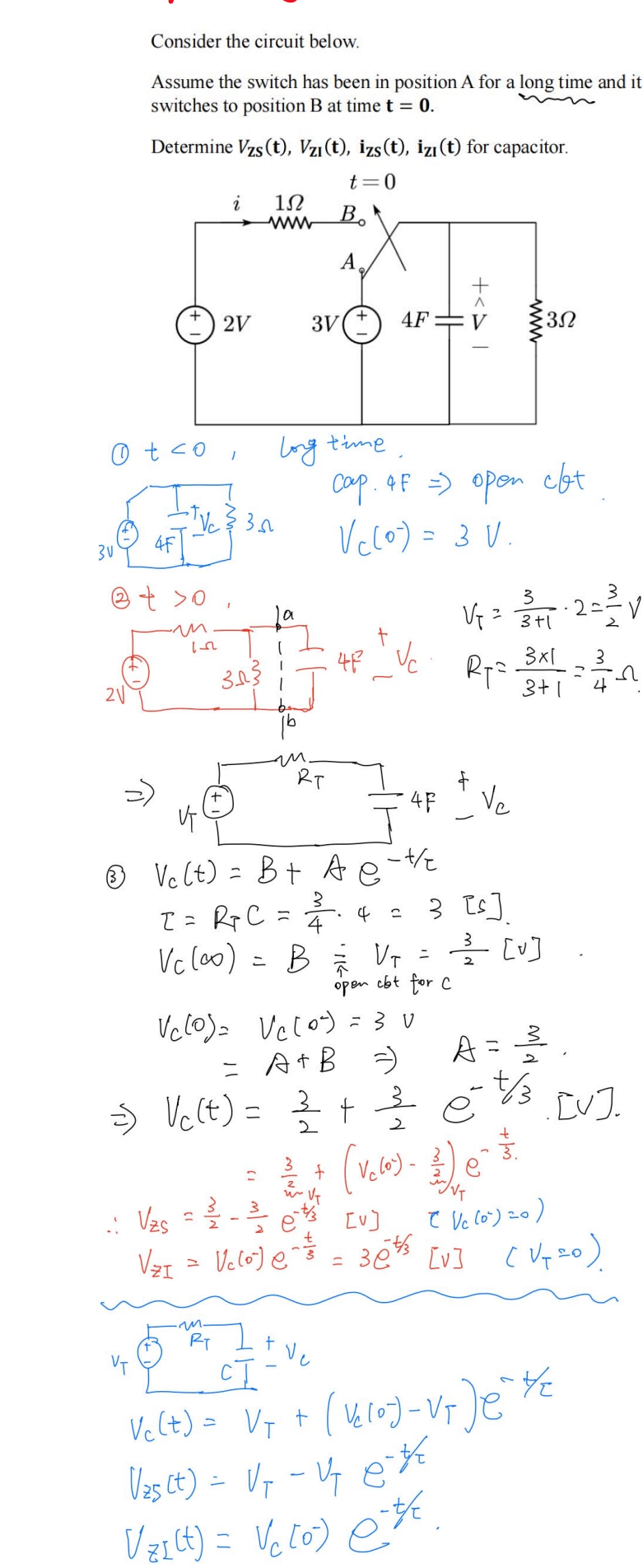

First Order RL → Thevenin to Norton

